

## OSCILLATOR

Defn:- The devices or circuit which is used to generate or produce the sinusoidal oscillations with desired change in frequency is called oscillator.

### Advantages of oscillators:-

- (i) It is a non rotating device.
- (ii) Due to absence of moving parts, the operation of oscillator is quite silent.
- (iii) An oscillator can produce the signal from small-freq. ( $50\text{ Hz}$ ) to large-freq. ( $> 100\text{ MHz}$ ).
- (iv) The frequency of oscillations can be easily changed by changing parameters.
- ~~(v)~~ **FIRMA BIAS** good frequency stability.
- (vi) It has very high efficiency.

TYPES OF OSCILLATOR:- Depending on the nature of op-oscillators are classified as

- (i) Sinusoidal oscillators

Notes By:-

- (ii) Non-sinusoidal oscillators

P. I. Amey P. Raut

(i) Sinusoidal oscillators:- The oscillators which generates sinusoidal oscillations with change in freq. are called sinusoidal oscillators.

(ii) Non-sinusoidal oscillators:- The oscillators which generates the non-sinusoidal waveform such as square, triangular are called non-sinusoidal oscillators.

Notes By:-

Prof. Amey P. Raut


## TYPES OF OSCILLATIONS:-

Damped oscillations

Undamped osci.


Damped oscillations:- the oscillations whose magnitude is changes with respect to time are called damped oscillations.

e.g.

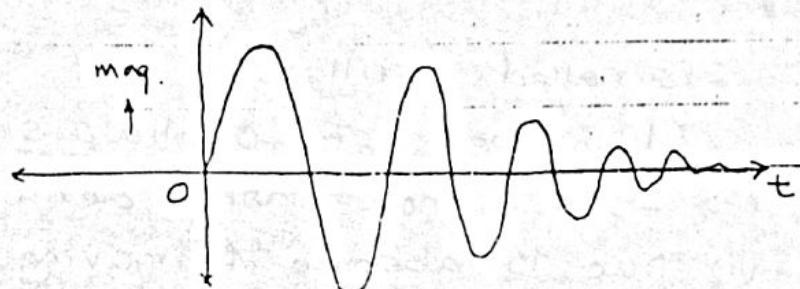

Undamped oscillations: The oscillations whose magnitude remains constant irrespective of increase the time are called undamped oscillations.


e.g.

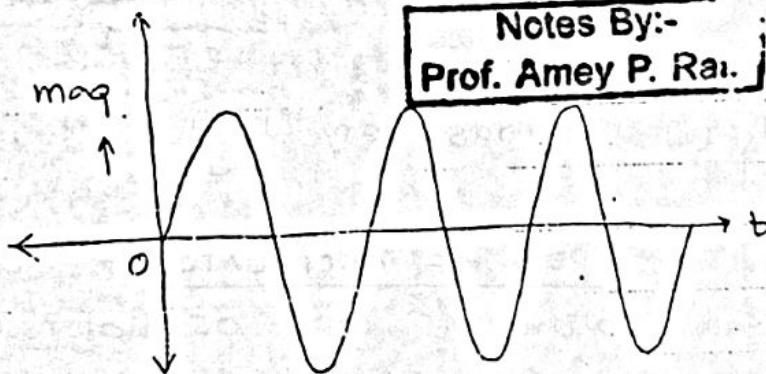

Notes By:-  
Prof. Amey P. Rai.

TANK CIRCUIT:- (oscillatory circuit):

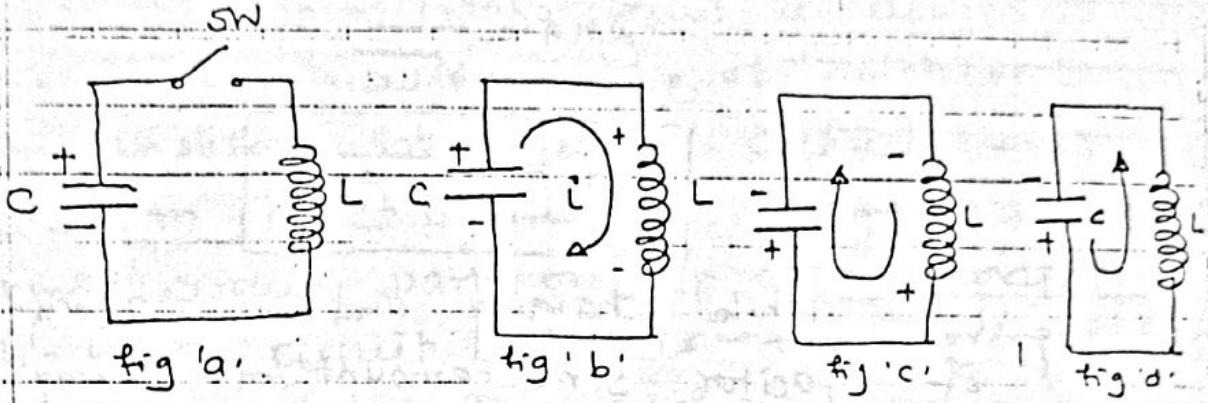It is a parallel combination of capacitor and inductor used to produce the oscillations with desired frequency. Consider inductor and cap. are connected in parallel through switch 'SW'. as shown.



Initially capacitor is charged towards its maximum value by using ext. dc source. When the capacitor is full charged switch 'SW' is closed so that capacitor will start discharging through inductor 'L' which stores the energy in it ( $E = \frac{1}{2} L I^2$ ). When capacitor is fully discharged, energy stored in inductor is max. Now, inductor starts supplying energy to the capacitor keeping the same dir. of current so that capacitor will start charging toward's its max. value with opposite polarity shown in fig 'c'. When energy of inductor decays completely, capacitor is fully charged. and again it will start discharging through the inductor in opposite dir. which will again store the energy in the inductor thus charging and discharging of capacitor will generate the oscillations with desired freq. and the freq. of oscillation can be calculated by -

$$X_L = X_C$$

$$\therefore \omega L = 1/\omega C$$

$$\therefore \omega^2 = \frac{1}{LC}$$

$$\therefore \omega = \frac{1}{\sqrt{LC}}$$

Notes By:  
Prof. Amey P. Raut

$$\text{But } \omega = 2\pi f$$

$$\therefore 2\pi f = \frac{1}{\sqrt{LC}}$$

$$\therefore f = \frac{1}{2\pi\sqrt{LC}}$$

While charging and discharging of capacitor some amount of energy will lost which will produce damped oscillations so that to recover the losses taking place in tank circuit it is necessary to provide feedback to the tank circuit.

**Notes By:-**  
**Prof. Amey P. Raut**

### BLOCK DIAGRAM OF OSCILLATOR:-


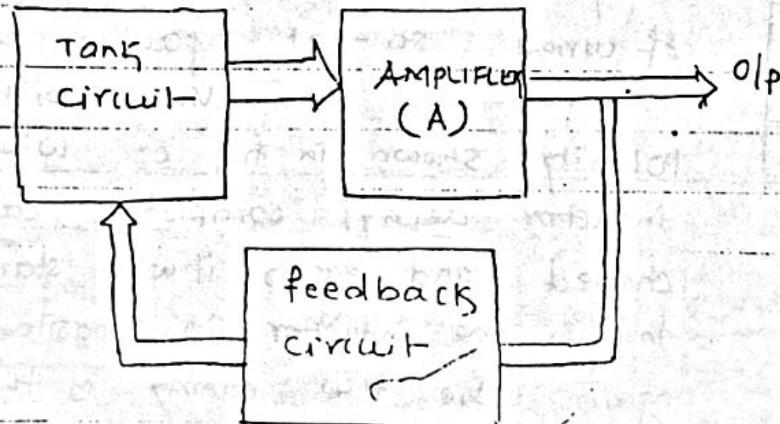


Fig shows the blocks diagram of oscillator it consists of tank circuit, amplifier and feedback circuit where tank circuit is used to produce the sinusoidal oscillations and with change in frequency.

the  
is  
and  
tanks  
the  
Phasing  
ray  
✓ BT  
crithe  
the - it  
(i) to  
(ii)  
(iii)

OR :-

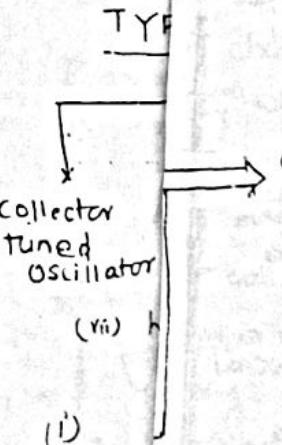

f  
rict  
T.  
duce  
with


the o/p of tank circuit is applied to the amplifier so that o/p of amplifier is in amplified form having desired level. and to overcome the losses - taking place in tank circuit, part of o/p is feed back to the tank circuit which is +ve having phase shift of  $0^\circ$  or  $360^\circ$ .

### BARKHAUSON CRITERION :-

Barkhausen criterion for the oscillator used to generate the desired oscillations state that -

- it requires +ve feedback.
- phase shift should be  $0^\circ$  or  $360^\circ$ .
- $B\Delta V = 1$ .

### TYPES OF SINE-SOIDS OSCILLATORS:-

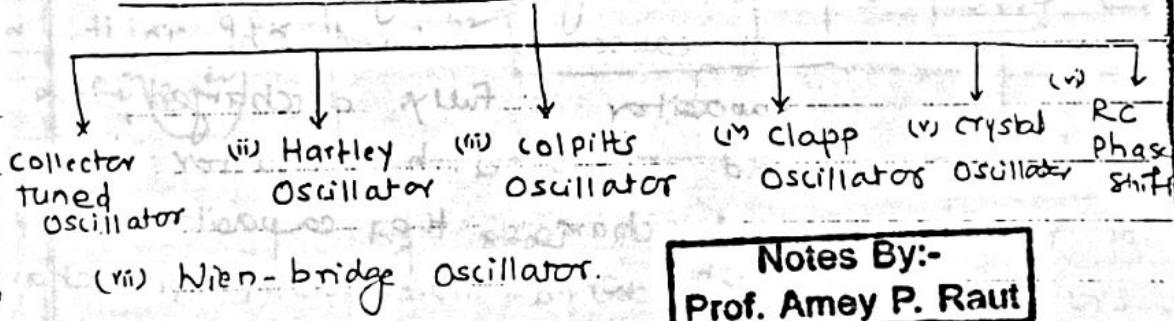

### (i) TUNED- COLLECTOR OSCILLATOR:-

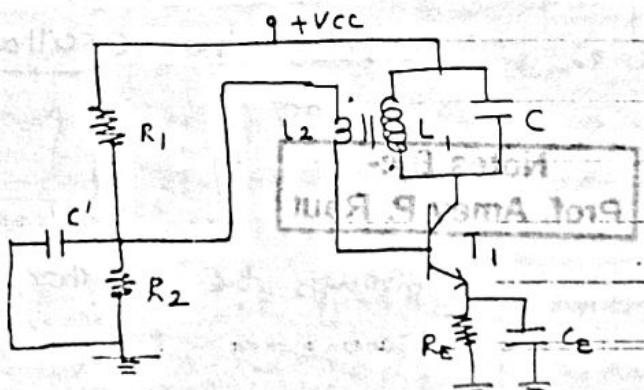


Fig shows the Collector tuned oscillator in which tank circuit forms by  $C$  and  $L_1$  connected at the collector of transistor and  $R_1$  and  $R_2$  is a voltage divider biasing resistors used to provide sufficient voltage at the base of transistor.  $C'$  and  $C_E$  are the by pass capacitors for resist  $R_2$  and  $R_E$  and  $L_2$  is used to provide the feedback for the tank circuit through the transistor as an amplifier.

When the circuit is energised by switching on the supply, the collector current starts increasing to the quiescent value. This current charges the capacitor  $C$ . When the capacitor is fully charged, it discharges through the inductor  $L_1$  which will cause to induced emf in it. When capacitor is fully discharged, the magnetic field produced by inductor will collapse and charge's the capacitor in opposite direction. When the capacitor will charge towards its max. value, it will again discharge through inductor  $L_1$ , thus it will produce the oscillations of desired frequency -

$$f = \frac{1}{2\pi \sqrt{LC}}$$

**Notes By:-**  
**Prof. Amey P. Raut**

When the capacitor is discharged through the inductor, by the mutual induction phenomenon emf is induced in the  $L_2$ .

which will again applied to the tank circuit through amplifier to recovery the losses taking place in tank circuit. Here tank circuit and transistor is used to provide the phase of  $360^\circ$  or  $0^\circ$ .

## (ii) HARTLEY OSCILLATOR :-

**Notes By:-**  
**Prof. Amey P. Raut**

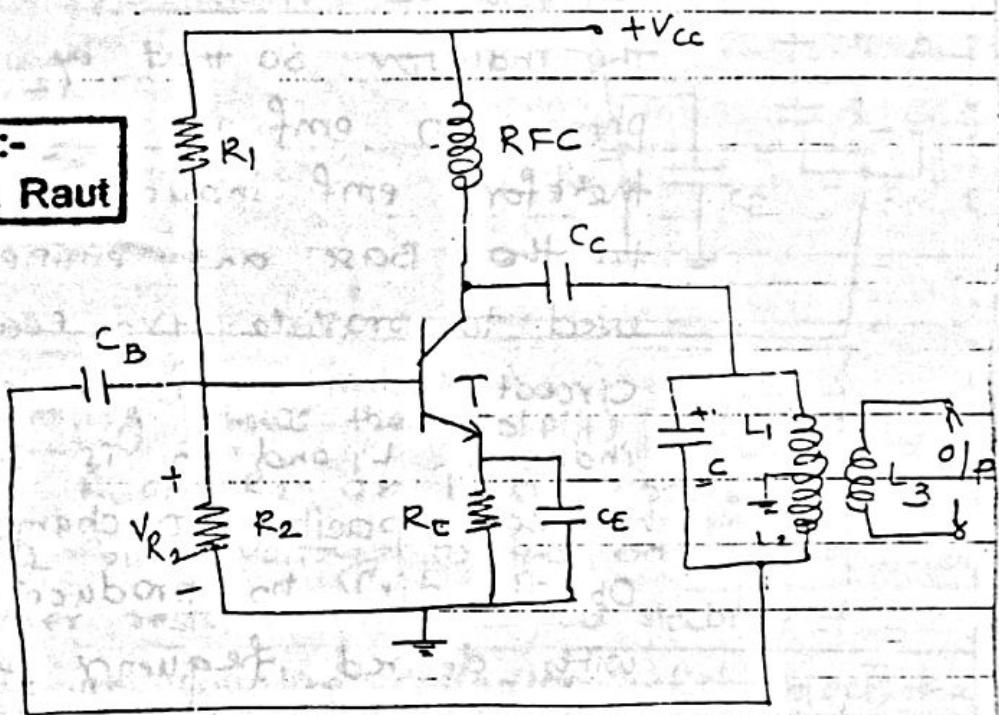


Fig shows the hartley oscillator in which  $R_1$  and  $R_2$  are the biasing resistors used to provide sufficient biasing voltage to the base of transistor.  $C_C$  and  $C_B$  are the coupling capacitors which blocks the d.c. current.  $R_E$  is used to improve the stability and  $C_E$  is a bypass capacitor for resistance  $R_E$ . Here  $R_{FC}$  is act as a load of transistor which is used to Neglect the effect of external magnetic field. the tank circuit formed by  $C$ ,  $L_1$  and  $L_2$  is

connected between the collector and the base of transistor.

When the circuit is energised by switching on the supply, collector current starts flowing through the circuit which charges the capacitor towards its max. value. When the capacitor is fully charged, it starts discharging through the inductor  $L_1$  and  $L_2$  which stores the energy in the inductor. So that by the self induction phenomenon emf is induced in  $L_1$  and  $L_2$ . Therefore emf induced in  $L_2$  is applied to the base and emitter of transistor used to provide +ve feedback to the tank circuit. When capacitor is fully discharged, inductor  $L_1$  and  $L_2$  is supplied energy to the capacitor to charge it again in opposite dirn. to produce the oscillation with desired frequency, which is measured across  $L_3$ .

Notes By:-  
Prof. Amey P. Raut

$$f = \frac{1}{2\pi\sqrt{LC}}$$

Where  $L = L_1 + L_2 + 2M$

Here tank circuit and transistor's is used to provide a phase shift of  $0^\circ$  or  $360^\circ$  to obtain desired oscillations.

the Base


biased by current which max.

is charged. inductor part in R induction L<sub>1</sub> and L<sub>2</sub>. If applied to transistor U<sub>b</sub> the tank edischarge energy gain in oscillation measured

is used  $40^\circ$  or  $360^\circ$

(iii)

### COLPITTS OSCILLATOR :-

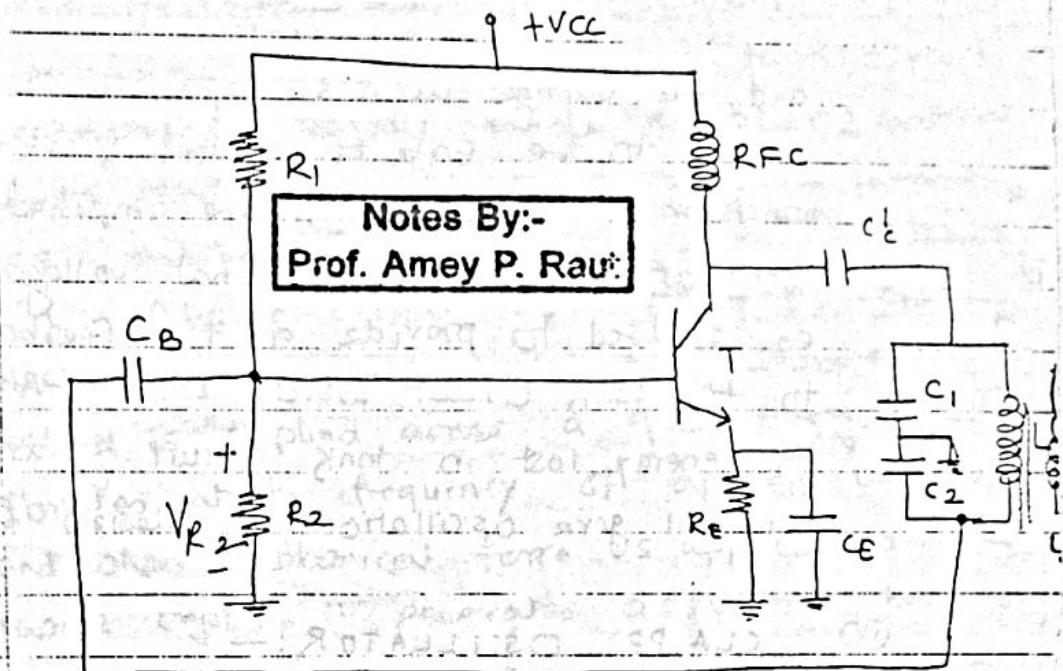

Notes By:- Prof. Amey P. Rau

Fig shows the Colpitts oscillator, in which R<sub>1</sub> and R<sub>2</sub> are biasing resistors used to provide bias voltage to the base of transistor. R<sub>E</sub> - emitter resistor improves the stability of circuit. C<sub>B</sub> and C<sub>c</sub> are coupling capacitor which blocks the d.c. current allows to pass to the a.c. signal. C<sub>c</sub> is a bypass capacitor for resistor R<sub>E</sub> and tank circuit which forms by C<sub>1</sub>, C<sub>2</sub> and L is connected bet' collector and Base of transistor and RFC is used to neglect the effect of external magnetic field and blocks the a.c. current.

When the circuit is energised by applying V<sub>cc</sub>, capacitors C<sub>1</sub> and C<sub>2</sub> charges towards its max. value. When the capacitors are fully charged, it will discharge through inductor L. which causes to produce the oscillations of

freq.


$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$\text{Where } C = \frac{C_1 C_2}{C_1 + C_2}$$

and the voltage across capacitor  $C_2$  is applied to the base to emitter junction of transistor which appear in the amplified form at [the collector] so that voltage of  $C_2$  is used to provide a +ve feedback to the tank circuit which will recover the energy lost in tank circuit. thus the ckt will give oscillations of desired freq.

#### (iv) CLAPP OSCILLATOR:-

**Notes By:-**  
**Prof. Amey P. Raut**

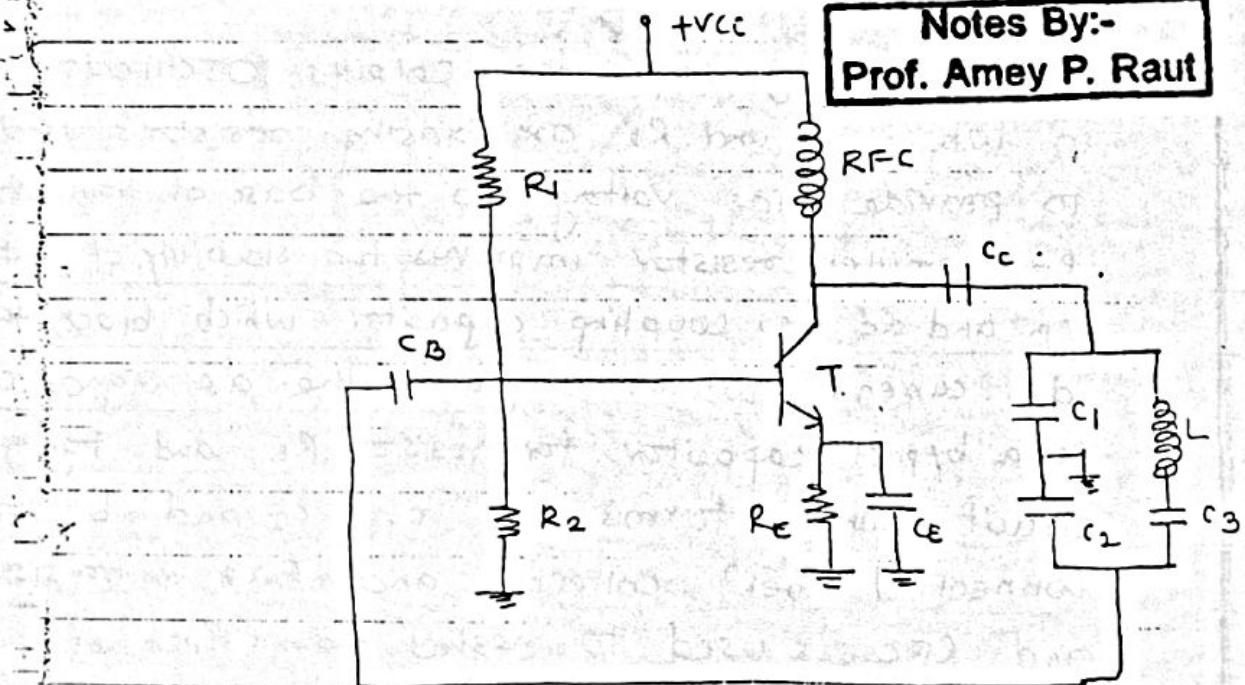


It is an improved version of Colpitt's oscillator in which extra capacitor  $C_3$  is connected in series with inductor of tank circuit to neglect the effect of variations of transistor parameters and stray capacitor.

(v) Crystal Oscillator :- It is basically a tuned oscillator. The crystal oscillator uses a piezoelectric crystal as a resonant tank circuit. The crystal is usually made of quartz material which provides high degree of accuracy and freq. stability.

Quartz crystal is working on piezo electric effect. Which states that when an a.c. voltage is applied across a quartz crystal, it vibrates at the frequency of applied voltage. And when mechanical force is applied to the quartz crystal it generates a voltage betn its two opposite faces which is called inverse piezo electric effect. It is available for the freq. of 15 kHz to 10 MHz.

**Notes By:-**  
**Prof. Amey P. Raut**


Equivalent ckt of crystal :-

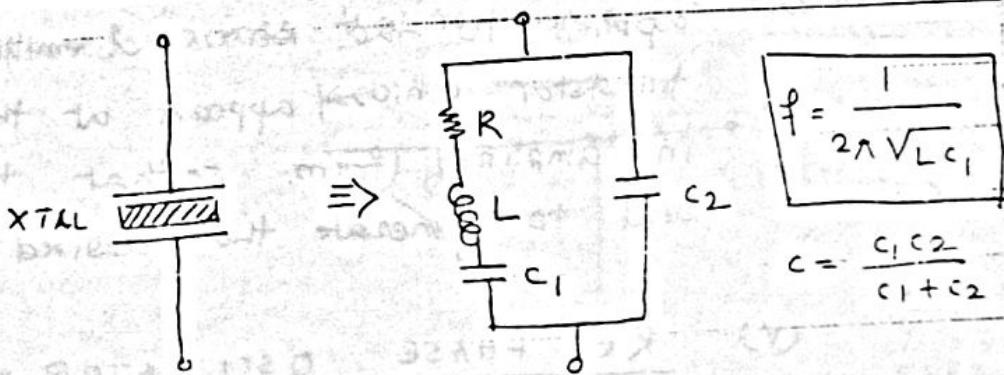

Crystal oscillator :- Below fig shows the crystal oscillator which consists of  $R_1$  and  $R_2$  as biasing resistors used to provide bias voltage at the base of transistor.  $R_E$  is used to improve the stability and  $C_E$  is a bypass capacitor for  $R_E$ . Here  $R_{FC}$  is used to provide for d.c. bias while

decoupling any a.c. signal on the power lines from affecting the o/p signal. crystal is connected bet' the collector and the Base of transistor through the capacitor 'C'.

**Notes By:-  
Prof. Amey P. Raut**

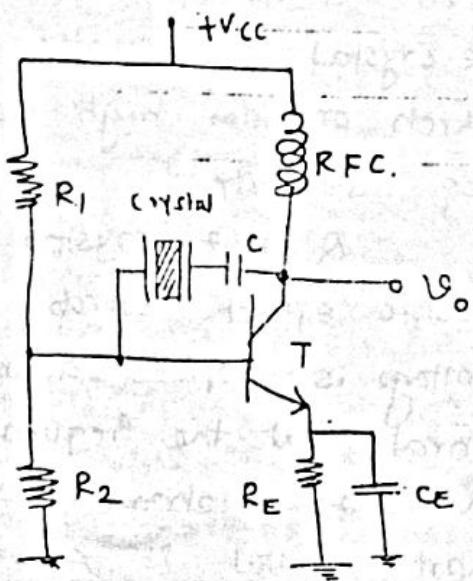


When the ckt is energised by applying  $V_{CC}$ . Voltage is appears across the crystal which will produces the oscillation of desired frequency. which will also applied to the Base and emitter of transistor which appears at the collector in amplified form. so that this ckt is used to generate the desired oscillations.

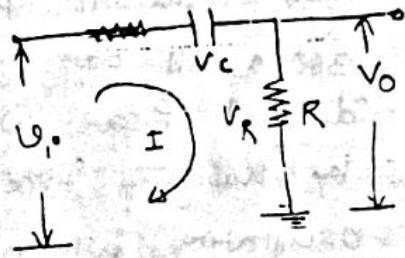(v) RC PHASE OSCILLATOR:- these oscillators employ resistors and capacitors are used to generate low or audio-freq. signals. Hence they are also called as audio freq. oscillators. the tuned (LC) oscillators are not suitable for low


is  
the  
capacitor

freq. because of size of inductor and capacitor  
we know that single stage ampl' not  
only amplifies the signal but produces the  
-ve feedback so that when part of o/p is  
feed back to the i/p it decreases the p/p which  
will not be able to generate the oscillation. so that  
to generate the oscillation's feedback required  
is +ve i.e. part of o/p should be applied  
to the i/p with proper phase shift which  
can be obtained by using R-C N/W's. Let  
us consider one R-C CKT -



Notes By:-  
Prof. Amey P. Raut

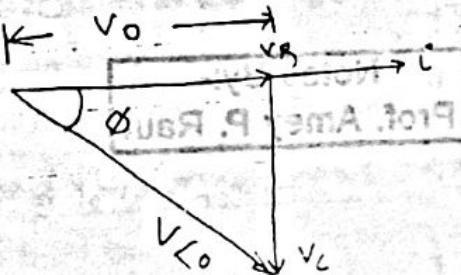Here Resistance and capacitance are connected  
in series across the voltage  $V_i$  and o/p is  
measured across the resistance.  $\therefore$  taking I as  
ref.



From the above vector diagram, we can say that  
R-C n/w is used to provide the phase shift  
bet'n i/p and o/p voltage. so that value of R  
c is adjusted such that it will give a  
phase shift of  $60^\circ$ .

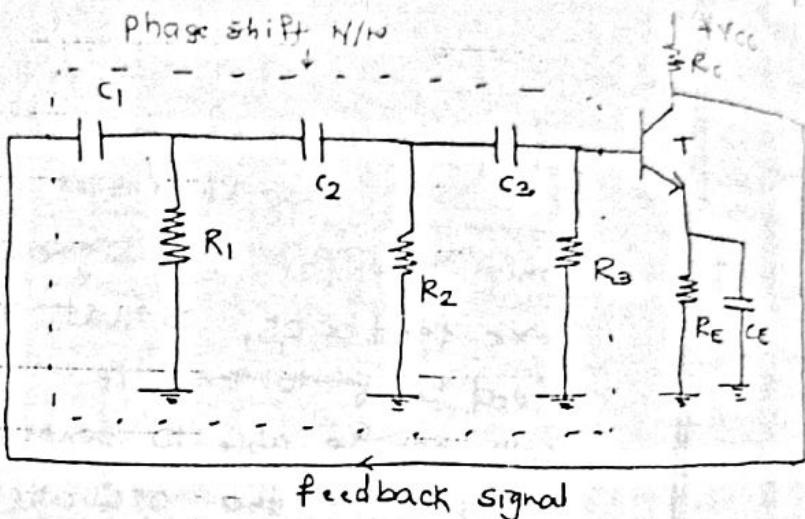


fig. shows the R-C phase shift oscillator. it consists of 3. R-C sections to give phase shift of  $180^\circ$  and transistor also provides a phase shift of  $180^\circ$  so that resultant phase shift of the N/H is  $360^\circ$  which will be provide the oscillations at desired freq. When the circuit is energized by applying  $V_{CE}$ . the circuit start oscillating which oscillation start due to minor variations in d.c. supply which will be maintained due to the feedback. the freq. of oscillations is given by

**Notes By:-**  
**Prof. Amey P. Raut**

$$f_0 = \frac{1}{2\pi\sqrt{R_C}} = 0.065$$



This consist of 3. R-C feedback now at the first stage the first section will give the signal to the second section to the third section.

At this time to raise the input voltage

$$\left| \frac{R_C}{R_1} \right| = 2^g$$

V<sub>CC</sub>V<sub>out</sub>

## (vi) WIEN BRIDGE OSCILLATOR:-

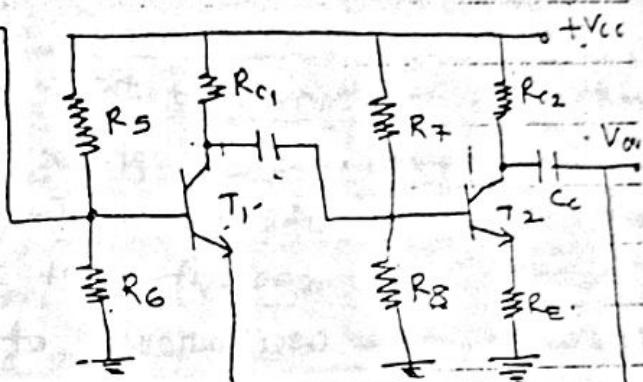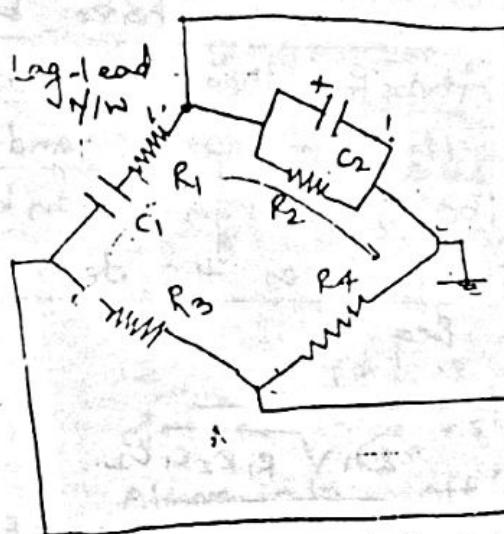

Notes By:-  
Prof. Amey P. Raut

fig. shows the Wien bridge oscillator which is used to overcome the disadvantage of R-C phase shift oscillator. When R-C phase shift is used to have a variable freq. circuit it is difficult to adjust equally the values of capacitors of phase-shift N/W. It consists of a two stage R-C coupled amplifier, which provides an phase shift of  $360^\circ$  or  $0^\circ$ . So that the feed back N/W has no need to produce any phase shift. The feed back network consists of  $C_1 - R_1$ ,  $C_2 - R_2$  (lead-lag N/W) and  $R_3 - R_4$  a voltage divider. The lead-lag network provides a positive feed back to the i/p of the first stage. The voltage divider provides -ve feed back to the emitter of  $T_1$  transistor.

When the circuit is energised by switching on the supply, a small random oscillation appearing at the base of  $T_1$  transistor are amplified, at its collector. These oscillations

are further amplified at the collector of  $T_2$  transistor. Since the oscillations at the collector of  $T_2$  transistor have been inverted twice, therefore these oscillations are in phase with i/p signal, and part of o/p is feedback through Wien bridge w/w. It till it produces the desired oscillation of freq.

Notes By:-  
Prof. Amey P. Rane

$$f_o = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$$

$$f_o = \frac{1}{2\pi R C} \quad \therefore R_1 = R_2 = R \\ \therefore C_1 = C_2 = C$$