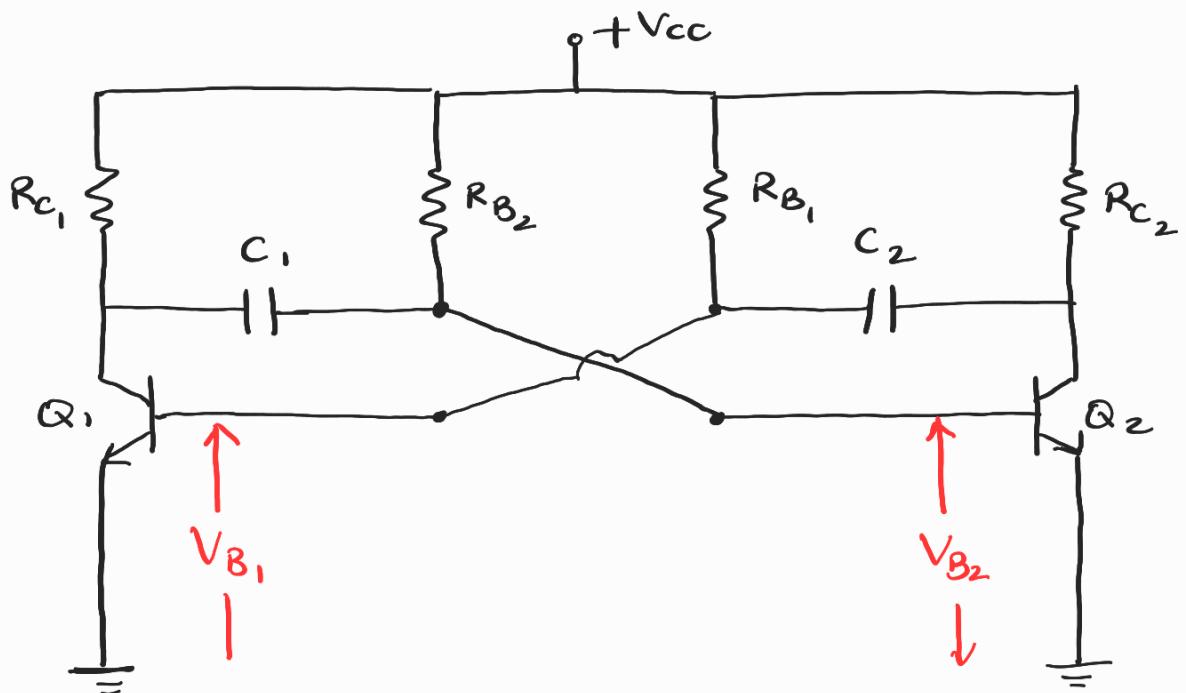


A STABLE MULTIVIBRATOR :-

An astable multivibrator is also called as free running relaxation oscillator. It is used for producing square wave.


Circuit Description:-



- 1.) There are 2 identical transistor Q_1 & Q_2 .
- 2.) Q_1 & Q_2 are cross coupled. i.e; the collector of Q_1 is connected to the base of Q_2 and similarly, collector of Q_2 is connected at the base of Q_1 .
- 3.) The amplifying stage provides 180° phase shift and C provides 180° .
Total phase shift is 360° or 0° . Thus a positive feedback is present.
- 4.) $R_B > R_C$ i.e $R_{B_1} > R_{C_1}$ & $R_{B_2} > R_{C_2}$.
- 5.) Either of the transistor conducts at a time due to imbalance in the circuit.

Working :-

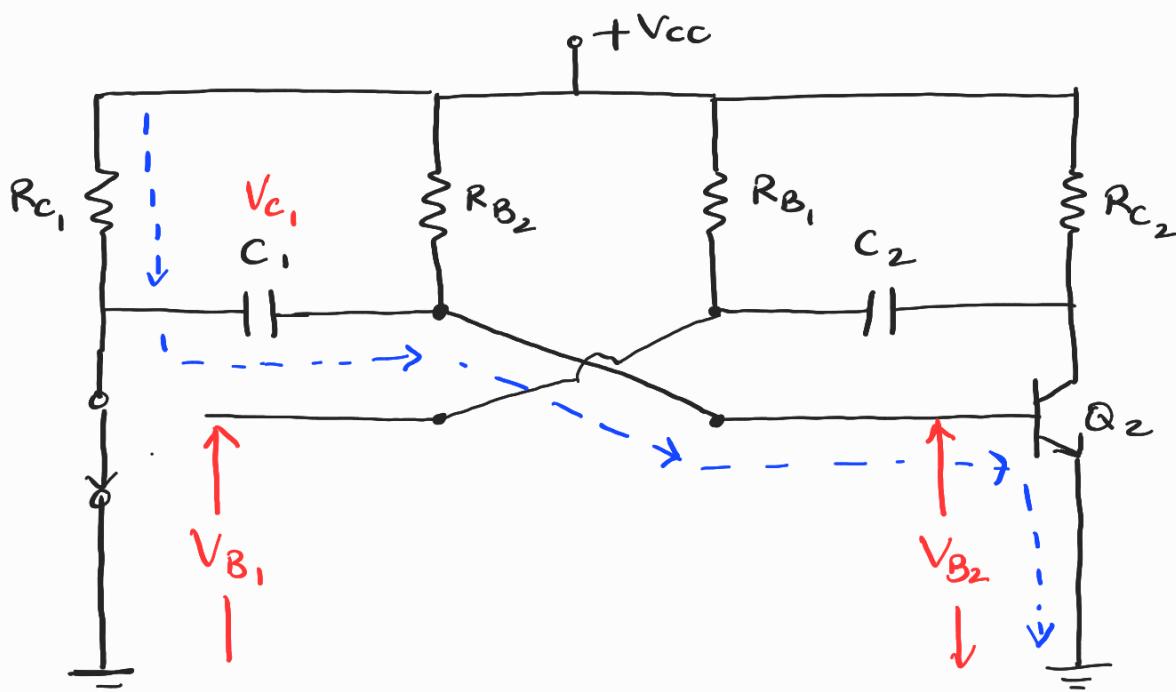
- 1.) Initially without the supply both the transistors Q_1 & Q_2 are in the 'OFF' state.
- 2.) When supply voltage V_{CC} is applied, one of the transistor will conduct.
- 3.) Let's say Q_1 is conducting. C_1 starts charging through R_{C_1} .



- 4.) As Q_1 is ON it acts as a close switch or short circuit path. The transistor is in the saturation region.
- 5.) The output is obtained at the collector of Q_1 , which is OV. Thus capacitor now connected to the ground.
- 6.) Due to this the capacitor starts charging in reverse direction. i.e., the capacitor C charges through R_{B_2} . $T' = R_{C_1} \cdot C_1$
- 7.) The collector is connected to the base of the Q_2 . Thus OV volt is connected at

the base of Q_2 which turns Q_2 OFF.

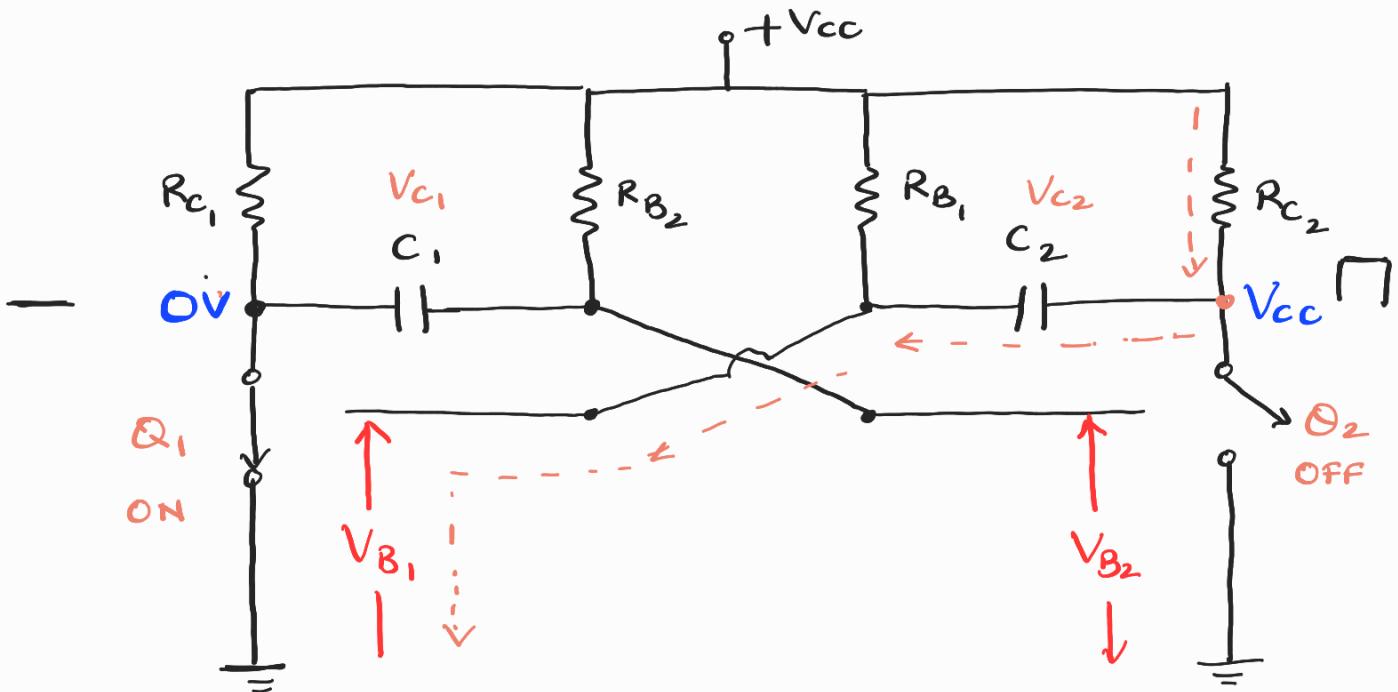- 8.) As Q_2 is OFF it acts as an open switch or open circuit path.
- 9.) The output at collector of Q_2 now is V_{cc} .



- 10.) The voltage across the capacitor C_2 is $V_{cc} - V_{BE}$. ($\because V_{cc} - V_{c2} - V_{BE} = 0$)
 $\therefore V_{c2} = V_{cc} - V_{BE}$).
- 11.) Q_1 turns 'ON' as the V_{BE} is greater than $0.7V$. $T_2 = R_B_1 C_2$.
- 12.) T_1 represents the duration for which the transistor Q_1 is ON and Q_2 OFF. Similarly time period T_2 represents for which the Q_2 is ON and Q_1 is OFF.
- 13.) Both time periods T_1 & T_2 depends upon charge of capacitors C_1 & C_2 . It can be

$$T_1 = 0.69 R_B_2 C_1$$


$$T_2 = 0.69 R_B_1 C_2$$

$$T = T_1 + T_2 = 0.69 (R_B_2 C_1 + R_B_1 C_2)$$

MONOSTABLE MULTIVIBRATOR:-

- ① It is also called one shot or univibrator and can be used to generate a gating pulse, whose width can be controlled.
- ② It provides single pulse of desired duration in response to an external trigger.

Circuit Description:-

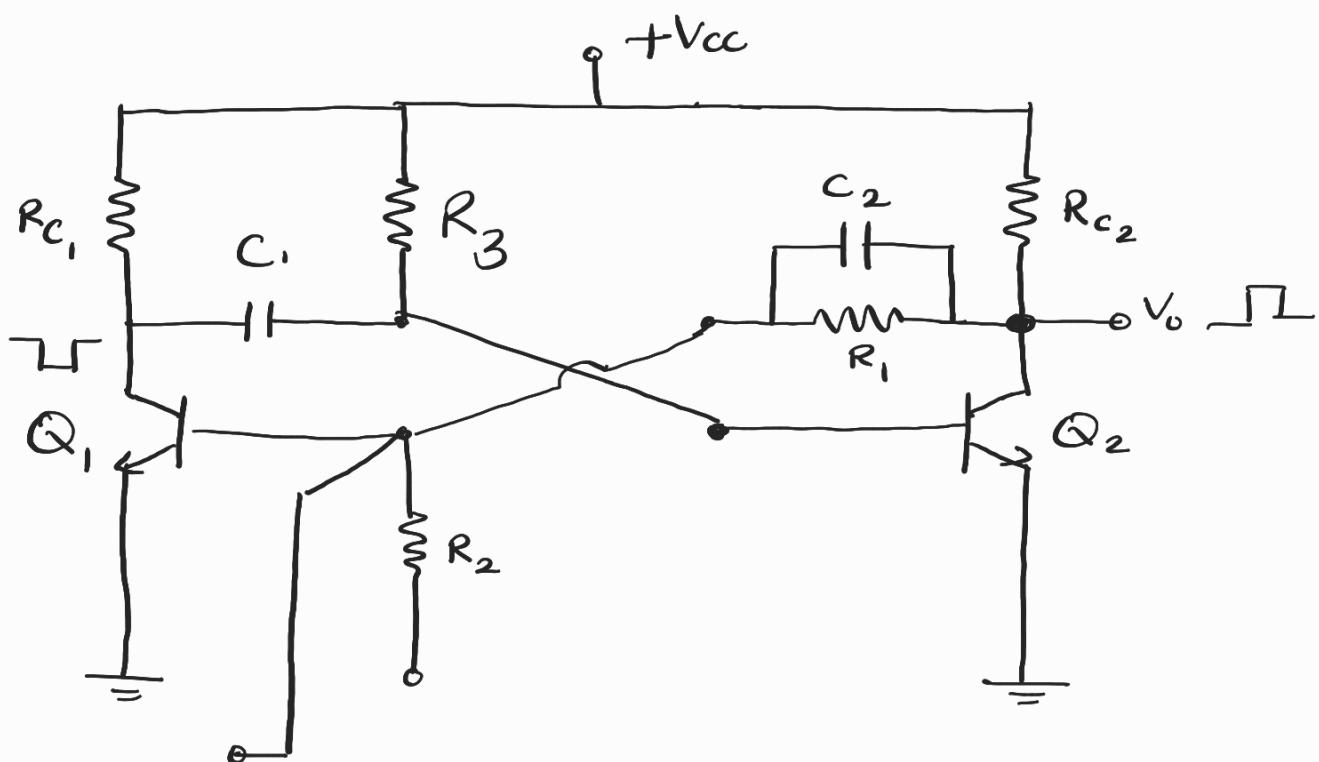

- ① It consists of 2 NPN transistors Q_1 & Q_2 , both are cross coupled.
- ② C_1 - commutating capacitor or speed up capacitor for making abrupt transitions b/w ON and OFF states.
- ③ The base of transistor Q_2 is returned to V_{CC} supply through resistor R_3 while

the base of Q_1 is connected to the -ve supply through a resistor R_2 .

- (4) The advantage of this biasing is that it keeps the transistor Q_1 off and Q_2 ON. This state is known as stable state of the monostable multivibrator.
- (5) The two outputs are complement of each other.


Working:-

- (1) When a 'tve' trigger pulse of sufficient amplitude is applied to the base of Q_1 it overrides the reverse bias provided by the V_{BB} supply and gives it a forward bias. Because of this Q_1 starts conducting.
- (2) The o/p at Q_1 is OV. This is coupled to the base of Q_2 which decreases the forward bias of transistor Q_2 .
- (3) Because of reduce forward bias Q_2 collector voltage starts increasing exponentially towards $\frac{V_{CC} \cdot R_1}{R_1 + R_{C_2}}$

$$\text{a time constant } T_2 = C_1 \cdot (R_1 || R_{C_2})$$

- (4) The rising V_{C_2} of Q_2 is coupled to the base of Q_1 through R_1 , where it further increase forward bias & Q_1 conducts more.

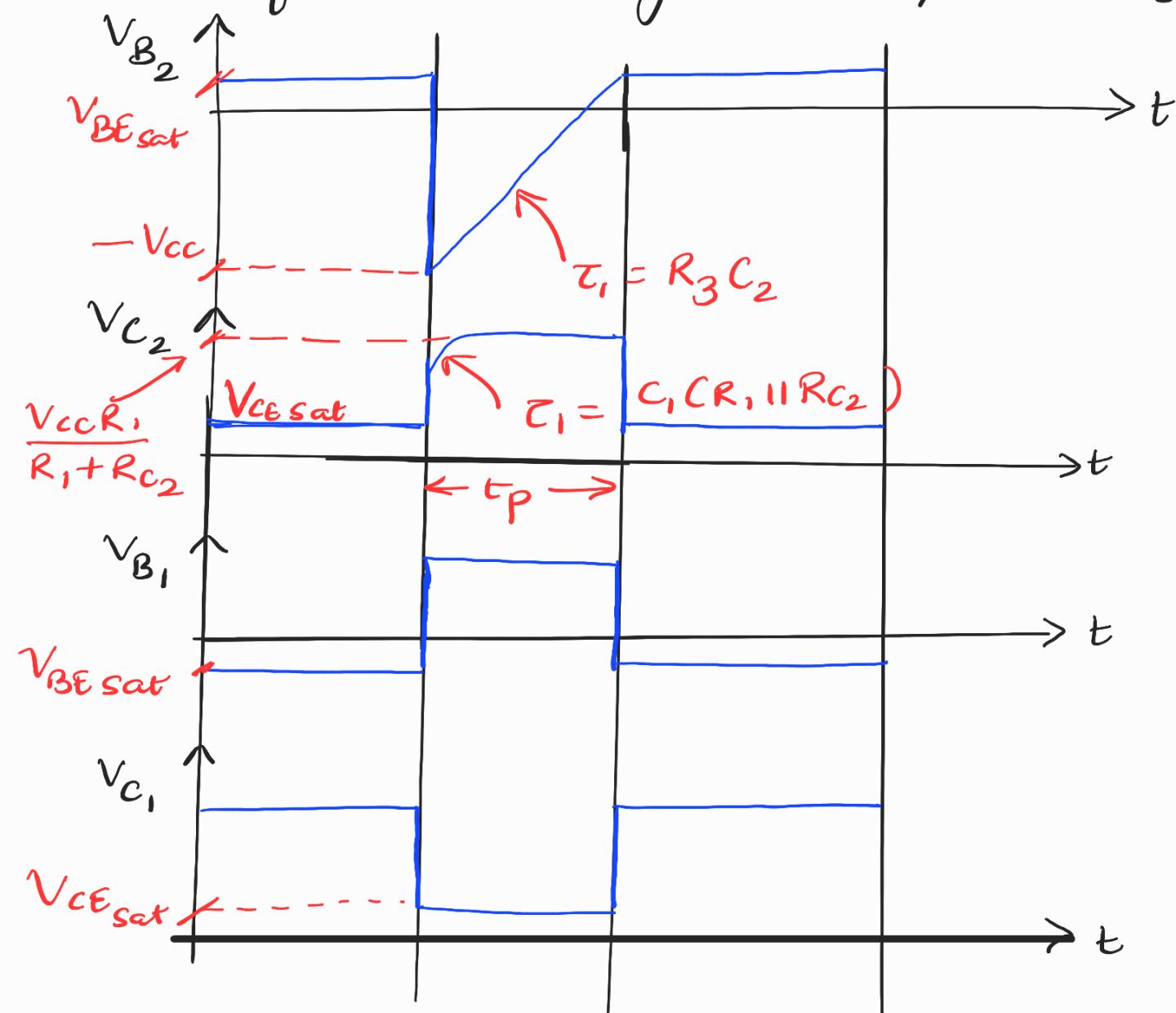
- (5) This action is cumulative because of the +ve feedback and V_{C_1} falls to $V_{CE(\text{sat})} = 0V$.
- (6) C_2 starts charging exponentially towards V_{CC} with a time constant $\tau_1 = C_2 R_3$.
- (7) C_1 charges further and Q_2 is turned ON and Q_1 OFF.
- (8) When Q_2 is ON, $V_{C_2} = V_{CE(\text{sat})}$ & Q_1 is OFF, $V_{C_1} = V_{CC}$.
 $\tau_3 = C_2 R_{C_1}$.
- (9) The pulse width at the collector of Q_1 & Q_2 is given as $t_p = 0.69 R_3 C_1$.



BISTABLE MULTIVIBRATOR:-

- ① It is also called flip-flop.
- ② It is used for counting and storing binary information in computer.
- ③ It has 2 stable states and can stay in any one of these 2 states, indefinitely, as long as the power is supplied.
- ④ It changes to the other state only when it receives a trigger (a short duration pulse) from outside.


Circuit Description :-


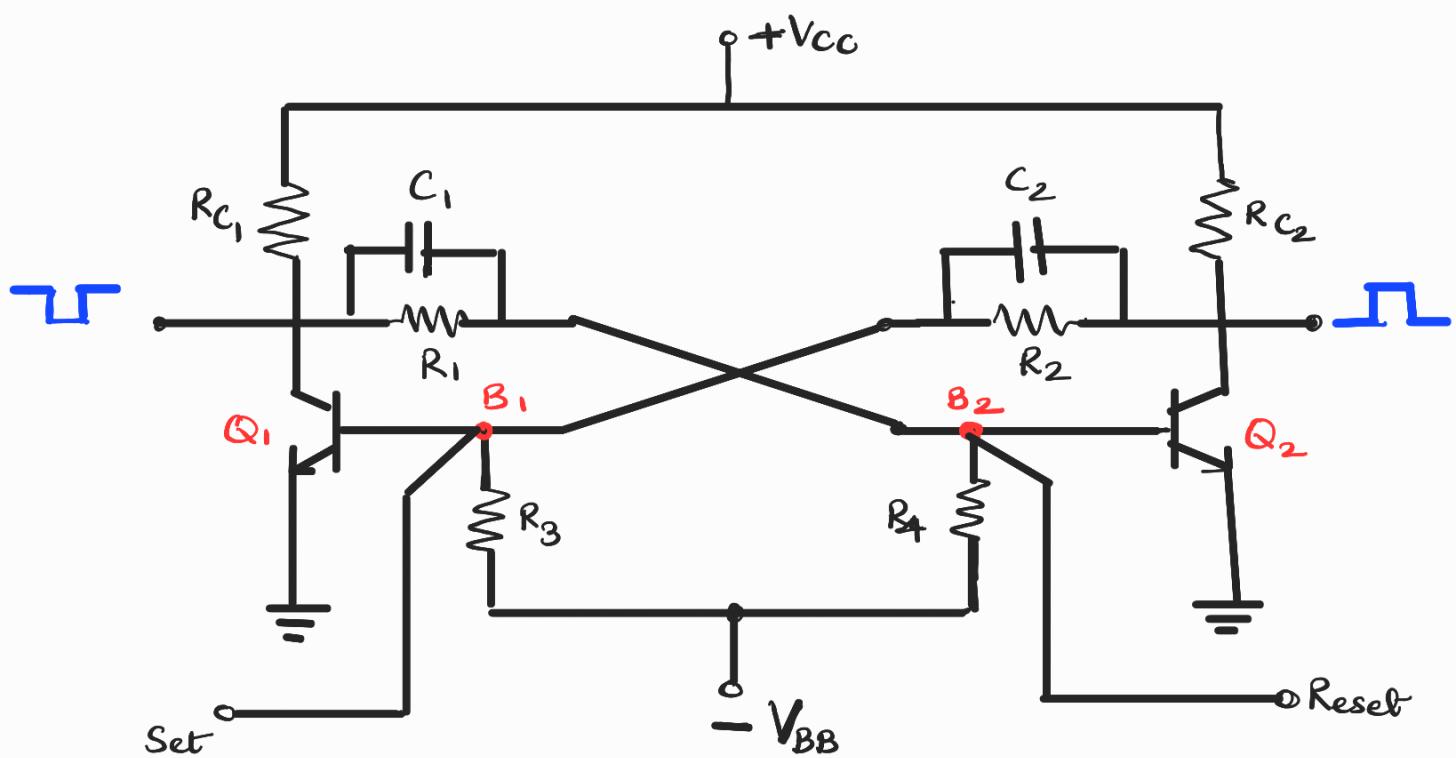


- 1.) 2 NPN transistors are cross coupled.
- 2.) C₁ & C₂ are speed up capacitors. Its function is to increase the speed of the circuit in making transition from one stable state to another stable state.
- 3.) The base resistors are connected to -V_{BB}.
- 4.) The o/p is obtained at the collector.

Working:-

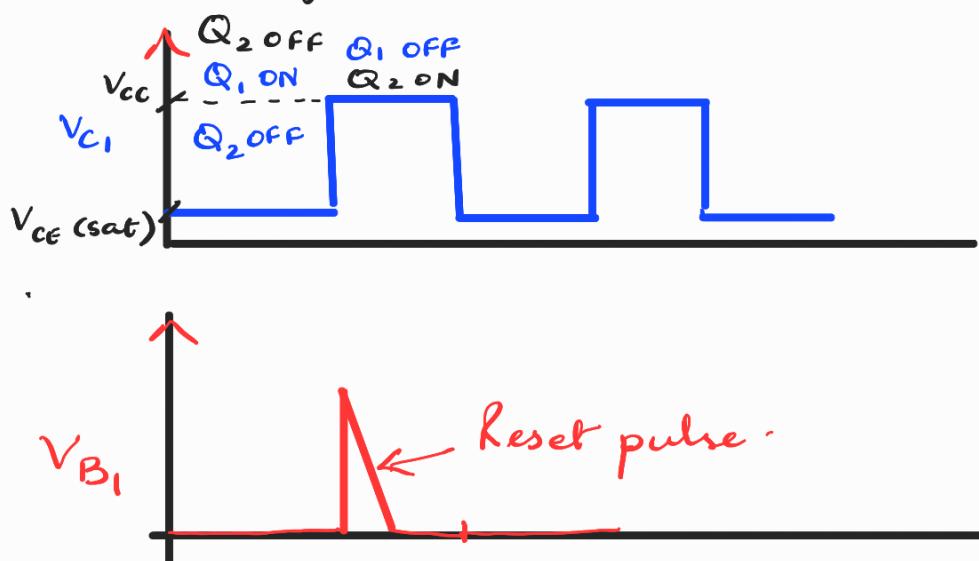- 1.) V_{cc} is supplied, one transistor will start conducting more than other. Then because of the feedback action, this transistor will be driven into saturation and other in cut off.
- 2.) Let us assume that the transistor Q_1 is in saturation (i.e ON) and Q_2 (i.e; OFF). This is the stable state of the ckt and will remain in this state till a next trigger pulse is applied from outside. **A negative pulse at the set I/P will turn OFF Q_1 and turn ON Q_2 .**
- 3.) Suppose a +ve pulse is applied at reset I/P. It will cause Q_2 to conduct and Q_1 turns OFF. Thus the circuit switches from one state to another stable state.
- 4.) Now, if a +ve pulse is applied to the set I/P it will switch the circuit back to its original state.



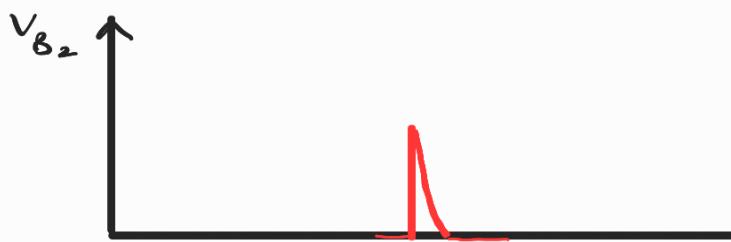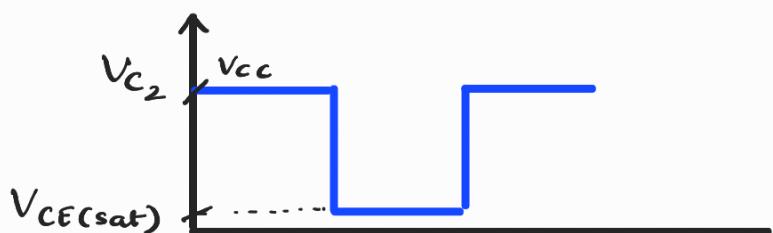

APPLICATIONS OF MULTIVIBRATORS

Used in variety of electronic circuit such as computer, control system and communication systems.
 Astable multivibrator - square waveform generators, voltage to frequency converters.

Monostable multivibrator - variable pulse width.

Bistable multivibrator - memory, counters.